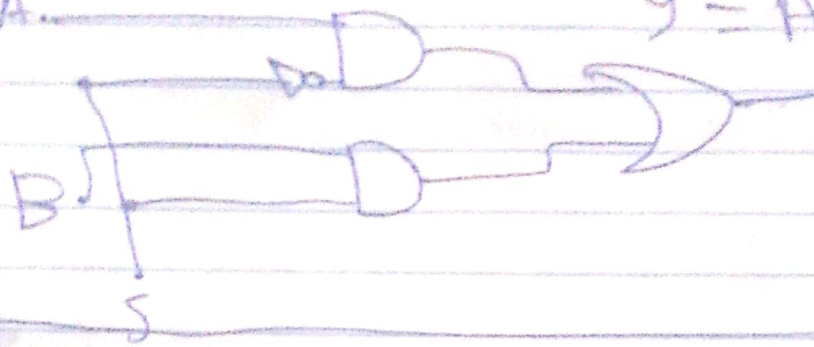


①


A

$$y = A\bar{B} + B\bar{A}$$




②

Not gate

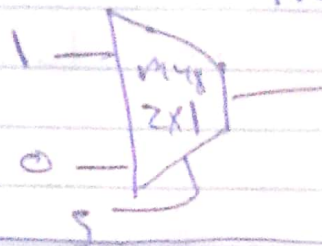


③

XOR gate

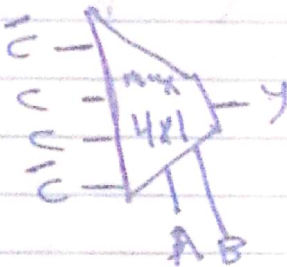



A	B	C	y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

④

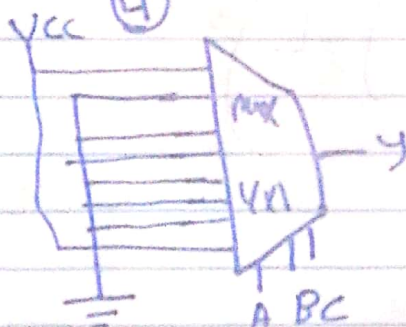
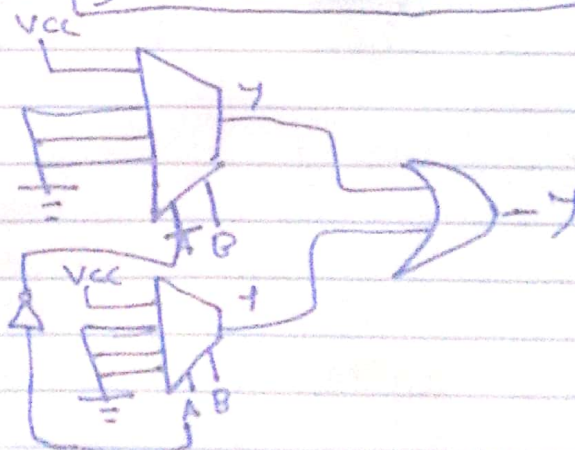
$$y = \bar{A}\bar{B}\bar{C} + A\bar{B}C$$



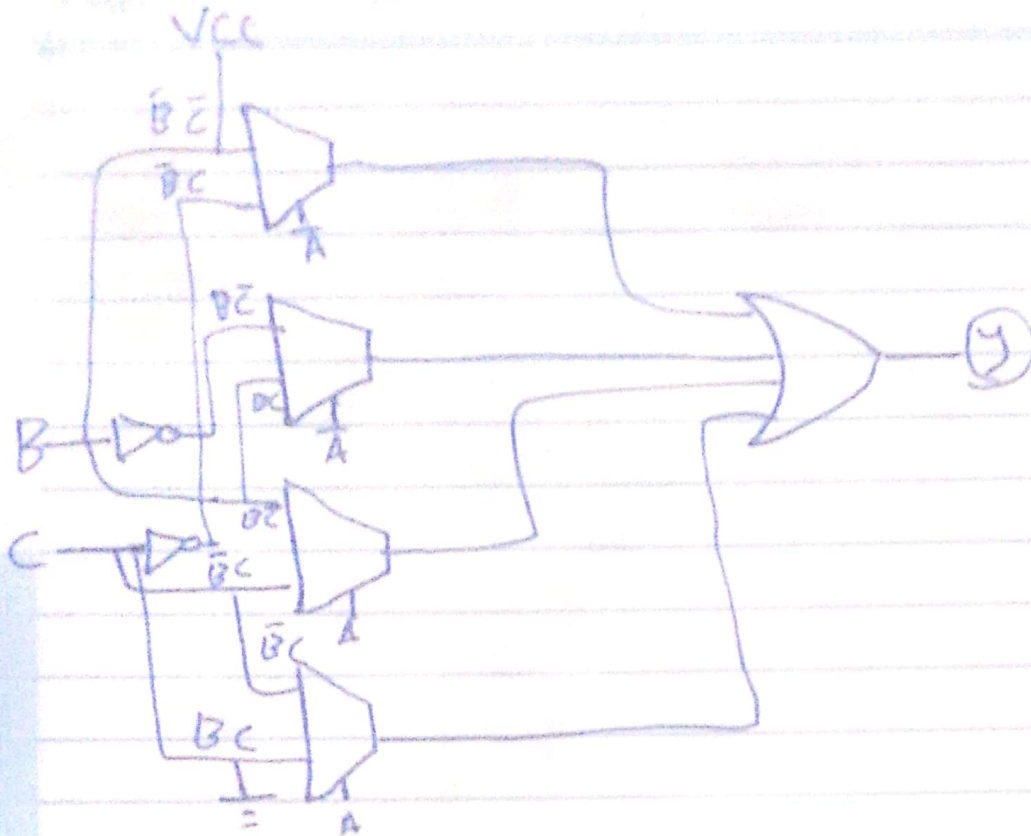

⑤ ① $C\bar{D} + \bar{C}D = \overline{C \oplus D}$, ② $F = A + (C \oplus D)$

⑥ ① $Y = \bar{C}\bar{D}$, ② $F = \bar{C}\bar{D}(A \oplus B) + \bar{A}\bar{B}$

⑦

